

Arquitecturas de Alto Desempenho

CRC Design

António Rui Borges

Application areas

Two basic application areas are considered

- message transmission
 - bit serial transmission
- data storage
 - parallel access.

Engineering problem to be dealt with

• how confidant can one be that the received message, or the retrieved data, is the same as the one that was transmitted, or stored?


Solution to be pursued

The message, or data, bits will be thought of to represent the coefficients of a polynomial to be operated in the Galois Field F_2 .

The remainder r(x), Cyclic Redundancy Checksum (CRC), of the polynomial division of $a(x) \times 10^8$ by $b(x) = x^8 + x^7 + x^5 + x^2 + x + 1$ is to be computed and attached to the message before transmission, or to the data before storage.

Upon message reception, or data retrieval, the polynomial $a(x) \times 10^8 - r(x)$ is to be divided again by b(x) and, if the remainder is not zero, an error should be signaled.


Parallel version

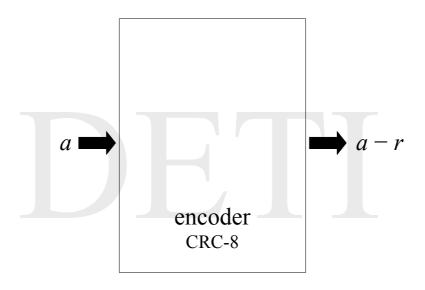

a - 16 bit word

r - 8 bit word

Parallel version

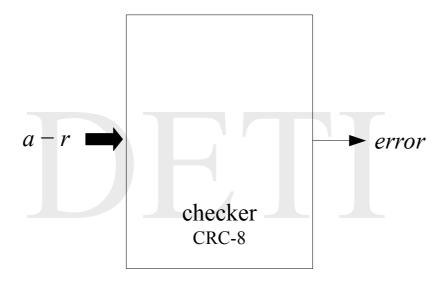


a - 16 bit word

r - 8 bit word

error – 1 bit word


Bit serial version

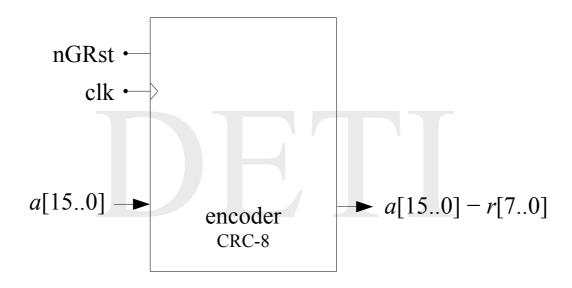

a - msb is inputted / outputted first

r – msb is outputted first

Bit serial version

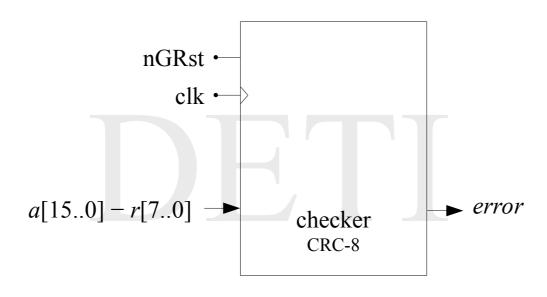

a – msb is inputted first

r – msb is inputted first



Basic approaches

The design may be approached through different methods, such as

- the division algorithm
- properties of the remainder.

$$a(x) \times x^{8} = q(x) \times b(x) + r(x)$$
where
$$b(x) = x^{8} + x^{7} + x^{5} + x^{2} + x + 1 \quad (CRC - 8 \text{ Bluetooth})$$

$$a(x) \times x^{8}$$

$$b(x)$$

$$r_1(x) \longrightarrow 0 \begin{picture}(20,0) \put(0,0){\line(1,0){160}} \put(0,0){\li$$

The computation can be simplified if we take into consideration that

- only the polynomial r(x) is required
- the last 8 coefficients of polynomial $a(x) \times x^8$ are known to be zero
- the form of polynomial b(x) is fixed and known.

Description of the computation as a recurring process

- there are 16 iteration steps
- initialization

$$r_{16,k} = a_{15+k-7}$$
, with $k = 0,1, \dots, 7$

• iteration step $(15 \ge i \ge 0)$

$$r_{i,8} = r_{i+1,7} \oplus q_i = r_{i+1,7} \oplus r_{i+1,7} = 0$$


$$k = 7, 5, 2, 1 \Rightarrow r_{i,k} = r_{i+1,7} \oplus r_{i+1,k-1}$$

$$k = 6, 4, 3 \Rightarrow r_{i,k} = r_{i+1,k-1}$$

$$k = 0 \land i \ge 8 \Rightarrow r_{i,0} = r_{i+1,7} \oplus a_{i-8}$$


$$k = 0 \land i < 8 \Rightarrow r_{i,0} = r_{i+1,7}$$

Two basic building blocks are needed.

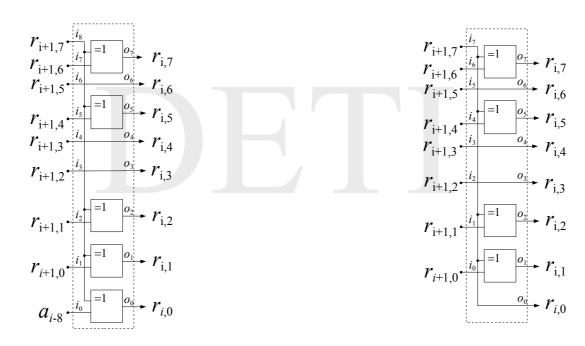

building block of type 1
9 inputs

building block of type 2 8 inputs

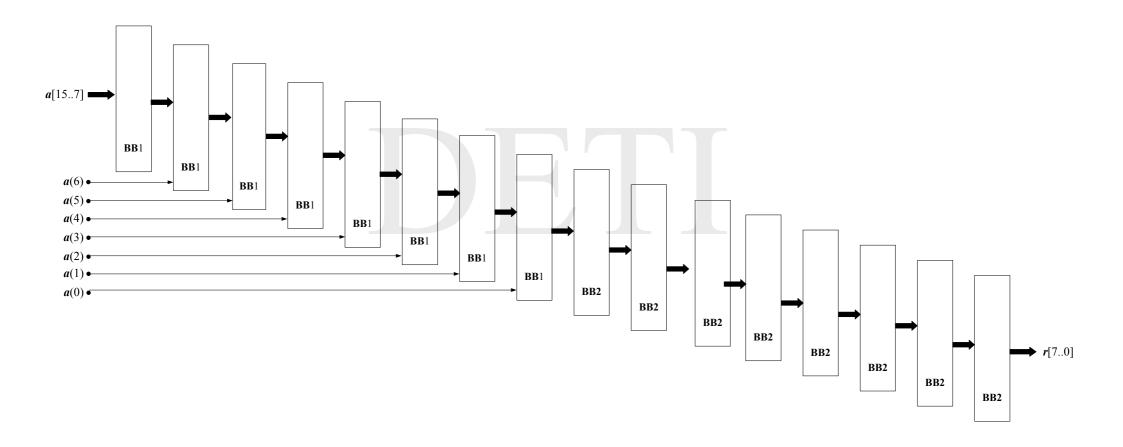

Output to input dependence + cost

iteration	
number	

	1 /	10	13	17	13	12	11	10
16	8000	4000	2000	1000	800	400	200	100
15	C000	2000	9000	800	400	8200	8100	8080
14	E000	9000	C800	400	8200	4100	4080	C040
13	7000	C800	E400	8200	4100	A080	2040	E020
12	B800	E400	F200	4100	A080	5040	9020	7010
11	5C00	F200	F900	A080	5040	2820	C810	B808
10	AE00	F900	FC80	5040	2820	9410	E408	5C04
9	5700	FC80	FE40	2820	9410	4A08	F204	AE02
8	AB80	FE40	7F20	9410	4A08	A504	F902	5701
7	55C0	7F20	3F90	4A08	A504	5282	FC81	AB80
6	2AE0	3F90	1FC8	A504	5282	A941	FE40	55C0
5	1570	1FC8	8FE4	5282	A941	D4A0	7F20	2AE0
4	0AB8	8FE4	47F2	A941	D4A0	6A50	3F90	1570
3	855C	47F2	A3F9	D4A0	6A50	3528	1FC8	0AB8
2	C2AE	A3F9	51FC	6A50	3528	9A94	8FE4	855C
1	6157	51FC	A8FE	3528	9A94	4D4A	47F2	C2AE
0	30AB	A8FE	547F	9A94	4D4A	26A5	A3F9	6157
	15 14 13 12 11 10 9 8 7 6 5 4 3 2	16 8000 15 C000 14 E000 13 7000 12 B800 11 5C00 10 AE00 9 5700 8 AB80 7 55C0 6 2AE0 5 1570 4 0AB8 3 855C 2 C2AE 1 6157	16 8000 4000 15 C000 2000 14 E000 9000 13 7000 C800 12 B800 E400 11 5C00 F200 10 AE00 F900 9 5700 FC80 8 AB80 FE40 7 55C0 7F20 6 2AE0 3F90 5 1570 1FC8 4 0AB8 8FE4 3 855C 47F2 2 C2AE A3F9 1 6157 51FC	16 8000 4000 2000 15 C000 2000 9000 14 E000 9000 C800 13 7000 C800 E400 12 B800 E400 F200 11 5C00 F200 F900 10 AE00 F900 FC80 9 5700 FC80 FE40 8 AB80 FE40 7F20 7 55C0 7F20 3F90 6 2AE0 3F90 1FC8 5 1570 1FC8 8FE4 4 0AB8 8FE4 47F2 3 855C 47F2 A3F9 2 C2AE A3F9 51FC 1 6157 51FC A8FE	16 8000 4000 2000 1000 15 C000 2000 9000 800 14 E000 9000 C800 400 13 7000 C800 E400 8200 12 B800 E400 F200 4100 11 5C00 F200 F900 A080 10 AE00 F900 FC80 5040 9 5700 FC80 FE40 2820 8 AB80 FE40 7F20 9410 7 55C0 7F20 3F90 4A08 6 2AE0 3F90 1FC8 A504 5 1570 1FC8 8FE4 5282 4 0AB8 8FE4 47F2 A941 3 855C 47F2 A3F9 D4A0 2 C2AE A3F9 51FC 6A50 1 6157 51FC A8FE 3528	16 8000 4000 2000 1000 800 15 C000 2000 9000 800 400 14 E000 9000 C800 400 8200 13 7000 C800 E400 8200 4100 12 B800 E400 F200 4100 A080 11 5C00 F200 F900 A080 5040 10 AE00 F900 FC80 5040 2820 9 5700 FC80 FE40 2820 9410 8 AB80 FE40 7F20 9410 4A08 7 55C0 7F20 3F90 4A08 A504 6 2AE0 3F90 1FC8 A504 5282 5 1570 1FC8 8FE4 5282 A941 4 0AB8 8FE4 47F2 A941 D4A0 3 855C 47F2 A3F9 D4A0	16 8000 4000 2000 1000 800 400 15 C000 2000 9000 800 400 8200 14 E000 9000 C800 400 8200 4100 13 7000 C800 E400 8200 4100 A080 12 B800 E400 F200 4100 A080 5040 11 5C00 F200 F900 A080 5040 2820 10 AE00 F900 FC80 5040 2820 9410 9 5700 FC80 FE40 2820 9410 4A08 8 AB80 FE40 7F20 9410 4A08 A504 7 55C0 7F20 3F90 4A08 A504 5282 6 2AE0 3F90 1FC8 A504 5282 A941 5 1570 1FC8 8FE4 5282 A941 D4A0	16 8000 4000 2000 1000 800 400 200 15 C000 2000 9000 800 400 8200 8100 14 E000 9000 C800 400 8200 4100 4080 13 7000 C800 E400 8200 4100 A080 2040 12 B800 E400 F200 4100 A080 5040 9020 11 5C00 F200 F900 A080 5040 2820 C810 10 AE00 F900 FC80 5040 2820 9410 E408 9 5700 FC80 FE40 2820 9410 4A08 F204 8 AB80 FE40 7F20 9410 4A08 A504 F902 7 55C0 7F20 3F90 4A08 A504 5282 FC81 6 2AE0 3F90 1FC8 A504

$$a_{15} \cdots a_0 \Rightarrow$$

- $a_{15} \cdots a_0^{\sharp} \rightarrow 1$, if the variable is present in the expression
 - 0, otherwise
- 72 x-or gates are needed.

Propagation delay dependence

iteration number

	pdr7	pdr6	pdr5	pdr4	pdr3	pdr2	pdr1	pdr0
16	0	0	0	0	0	0	0	0
15	1	0	1	0	0	1	1	1
14	2	1	2	0	1	2	2	2
13	3	2	3	1	2	3	3	3
12	4	3	4	2	3	4	4	4
11	5	4	5	3	4	5	5	5
10	6	5	6	4	5	6	6	6
9	7	6	7	5	6	7	7	7
8	8	7	8	6	7	8	8	8
7	9	8	9	7	8	9	9	8
6	10	9	10	8	9	10	10	9
5	11	10	11	9	10	11	11	10
4	12	11	12	10	11	12	12	11
3	13	12	13	11	12	13	13	12
2	14	13	14	12	13	14	14	13
1	15	14	15	13	14	15	15	14
0	16	15	16	14	15	16	16	15

• 16 x-or propagation time delays in the worst case.

Properties of the remainder - 1

$$[a(x) \times x^{8}] \mod b(x) = \left[\left(\sum_{n=0}^{15} a_{n} \times x^{n} \right) \times x^{8} \right] \mod b(x) =$$

$$= \left(\sum_{n=0}^{15} a_{n} \times x^{n+8} \right) \mod b(x) = \sum_{n=0}^{15} \left[a_{n} \times \left[x^{n+8} \mod b(x) \right] \right]$$

where
$$b(x) = x^8 + x^7 + x^5 + x^2 + x + 1$$
 (CRC-8 Bluetooth)

Properties of the remainder - 2

$$x^{8} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{7} + x^{5} + x^{2} + x + 1$$

$$x^{9} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{7} + x^{6} + x^{5} + x^{3} + 1$$

$$x^{10} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{6} + x^{5} + x^{4} + x^{2} + 1$$

$$x^{11} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{7} + x^{6} + x^{5} + x^{3} + x$$

$$x^{12} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{6} + x^{5} + x^{4} + x + 1$$

$$x^{13} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{7} + x^{6} + x^{5} + x^{2} + x$$

$$x^{14} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{6} + x^{5} + x^{3} + x + 1$$

$$x^{15} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{7} + x^{6} + x^{4} + x^{2} + x$$

$$x^{16} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{3} + x + 1$$

$$x^{17} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{4} + x^{2} + x$$

$$x^{18} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{5} + x^{3} + x^{2}$$

$$x^{19} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{6} + x^{4} + x^{3}$$

$$x^{20} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{6} + x^{4} + x^{3}$$

$$x^{20} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{7} + x^{5} + x^{2} + x + 1$$

$$x^{21} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{7} + x^{5} + x^{2} + x + 1$$

$$x^{22} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{7} + x^{6} + x^{2} + x + 1$$

$$x^{22} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{6} + x^{4} + x$$

$$x^{23} \mod (x^{8} + x^{7} + x^{5} + x^{2} + x + 1) = x^{6} + x^{4} + x$$



Properties of the remainder - 3

$$\begin{split} \left(\sum_{n=0}^{15} a_n \times x^{n+8}\right) & mod \ \left(x^8 + x^7 + x^3 + x^2 + x + 1\right) = \\ &= \left(a_0 \oplus a_1 \oplus a_3 \oplus a_5 \oplus a_7 \oplus a_{12} \oplus a_{13}\right) \times x^7 + \\ &+ \left(a_1 \oplus a_2 \oplus a_3 \oplus a_4 \oplus a_5 \oplus a_6 \oplus a_7 \oplus a_{11} \oplus a_{13} \oplus a_{15}\right) \times x^6 + \\ &+ \left(a_0 \oplus a_1 \oplus a_2 \oplus a_3 \oplus a_4 \oplus a_5 \oplus a_6 \oplus a_{10} \oplus a_{12} \oplus a_{14}\right) \times x^5 + \\ &+ \left(a_2 \oplus a_4 \oplus a_7 \oplus a_9 \oplus a_{11} \oplus a_{12} \oplus a_{15}\right) \times x^4 + \\ &+ \left(a_1 \oplus a_3 \oplus a_6 \oplus a_8 \oplus a_{10} \oplus a_{11} \oplus a_{14}\right) \times x^3 + \\ &+ \left(a_0 \oplus a_2 \oplus a_5 \oplus a_7 \oplus a_9 \oplus a_{10} \oplus a_{13}\right) \times x^2 + \\ &+ \left(a_0 \oplus a_3 \oplus a_4 \oplus a_5 \oplus a_6 \oplus a_7 \oplus a_8 \oplus a_9 \oplus a_{13} \oplus a_{15}\right) \times x + \\ &+ \left(a_0 \oplus a_1 \oplus a_2 \oplus a_4 \oplus a_6 \oplus a_8 \oplus a_{13} \oplus a_{14}\right) \end{split}$$

- 58 x-or gates are needed
- 9 x-or propagation time delays in the worst case.

Parallel implementation

Following one of the approaches that were described, or some other one that you may devise

- elicit common operations to reduce gate count
- perform them in parallel to reduce time propagation delays.

Bit serial implementation

Following one of the approaches that were described, or some other one that you may devise

- elicit common operations in order to specify the data path
- design the control section so that the bit sequence may proceed smoothly through the data path.